JOEL NINAN JOHNSON
IBM19CS199

06/01/21

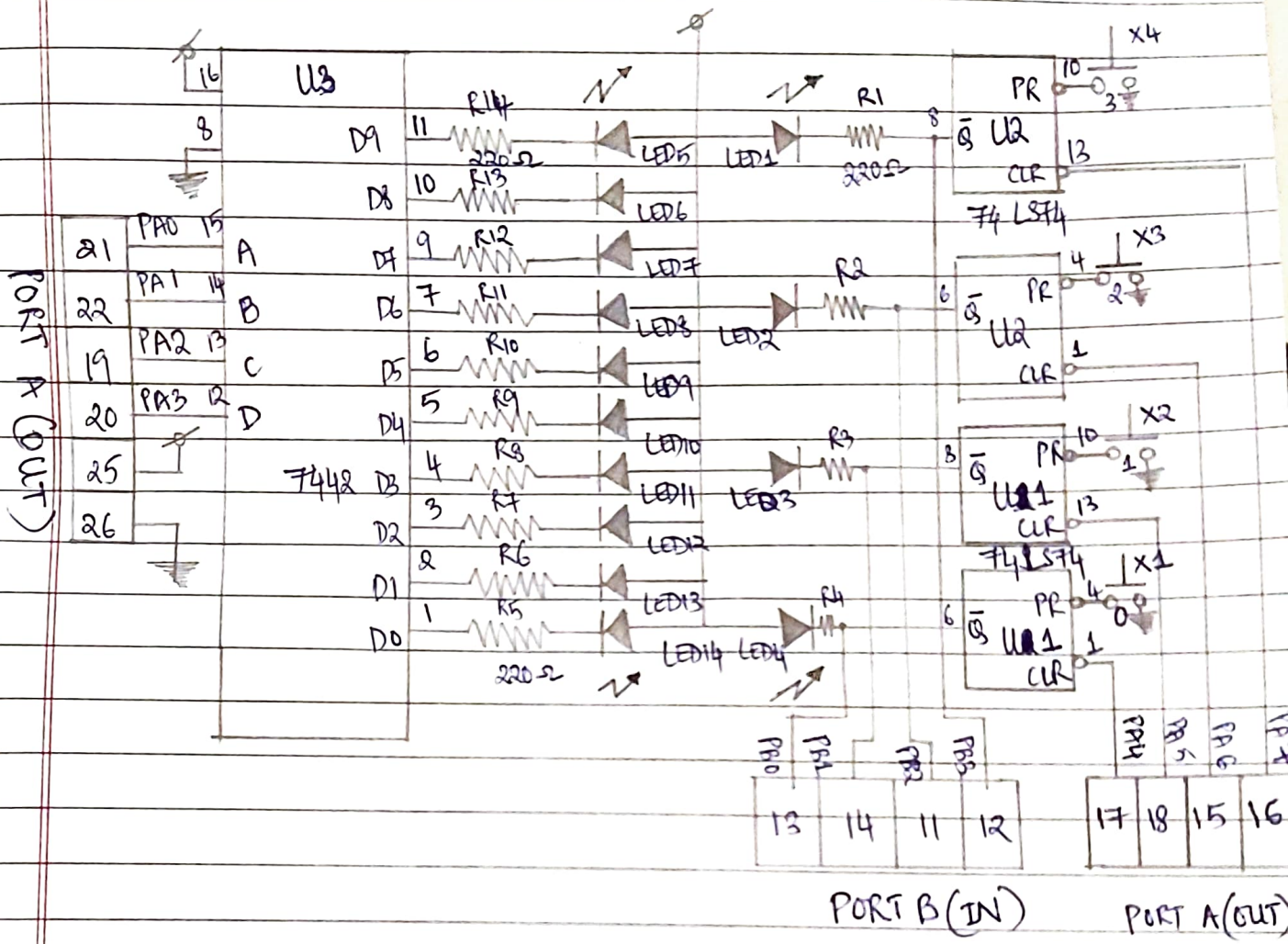

CIRCUIT DIAGRAM